

NPTEL Workshop: Homework 6 (Bonus)

Wadhvani Electronics Lab, IIT Bombay

13 July, 2022

1 Problem statement


Consider the following Sequence generator which generates a certain sequence upon every input clock pulse and on reset the sequence will go into default sequence i.e 6 in this case.

Design and implement both structural and behavioral below sequence generator and Perform RTL and Gate level simulation and scanchain with the given TRACEFILE.

Note: The reset is asynchronous in nature i.e reset effects the output sequence irrespective of the input clock arrival.

Inputs: Reset, clock

Output(3 bit):Y2Y1Y0

 

Tracefile format: (< reset >< clock > < y2y1y0 > < MaskBits >) Tracefile